



POLITECNICO DI TORINO

DIGITAL SYSTEMS ELECTRONICS
A.A. 2018/2019

PROF. G. MASERA

Lab 01

19 Mar 2019

Berchialla Luca	236032
Laurasi Gjergji	238259
Mattei Andrea	233755
Lombardo Domenico Maria	233959

1 Controlling the LEDs

2 2-to-1 Multiplexer

As figure 1 shows we are implementing a 2-to-1 Multiplexer using a structural approach. Since its internal implementation is pretty trivial we will not discuss it any further.

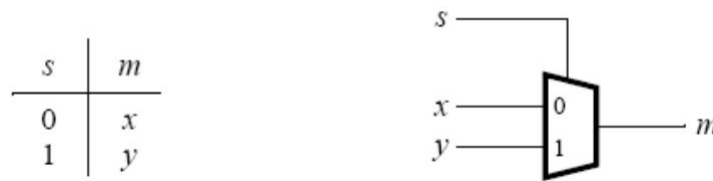


Figure 1: multiplexer + truth table

Its VHDL code has been written under Quartus prime. Then a testbench was developed under modelsim. In the testbench we fixed the two multiplexed inputs and then varying the selection bit we checked the behaviour.

After the simulation was successful we imported the pin assignments into Quartus prime and after compiling and loading it on the board we verified the actual behaviour.

3 5-to-1 Multiplexer

We're now interested in designing the circuit shown in figure 2, where the output signal can be chosen between 5 different input signals with a 3 bit control signal as shown in the truth table.

The circuit model has been implemented using a behavioural approach, that leads to a faster but less customizable solution to design a 5 to 1 MUX.

The circuit has been proved to work thanks to a testbench simulation, checking the correspondence of input-output following the already cited truth table.

Finally the vhd code has been loaded into the hardware fpga showing positive results as expected by simulation.

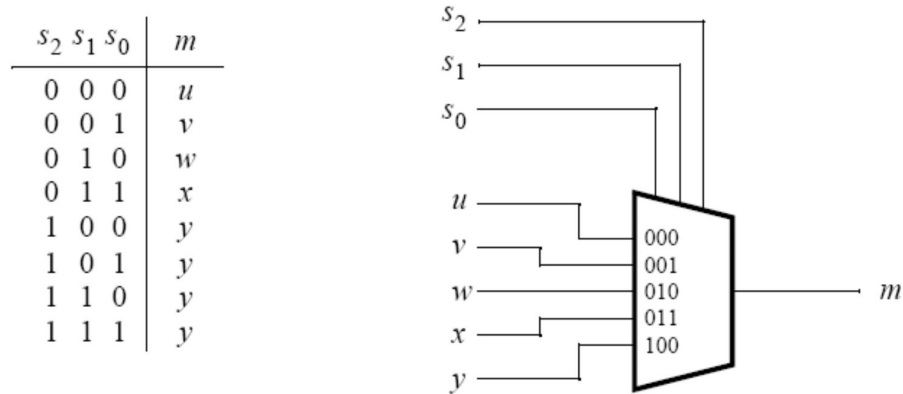


Figure 2: multiplexer + truth table