

Politecnico di Torino

DIGITAL SYSTEMS ELECTRONICS A.A. 2018/2019

Prof. G. Masera

Lab 02

24 Mar 2019

Berchialla Luca	236032
Laurasi Gjergji	238259
Mattei Andrea	233755
Lombardo Domenico Maria	233959

Lab 02

1 Controlling a 7-segments display

Figure 1 shows a 7-segment decoder module whose input bits C2C1C0 drive a 7 segment display through the bits $HEX0_0 -> HEX0_6$

 


Figure 1: 7-segment decoder + display

Figure 2 shows the truth table to be implemented for the 7-segment decoder. As shown just the characters HELO will be implemented. The sequent logical states can be easily derived from the table:

$$\begin{split} HEX6 &= \overline{C2} \cdot \overline{C1} \\ HEX5 &= \overline{C2} \\ HEX4 &= \overline{C2} \\ HEX3 &= \overline{C2} \cdot (C0 + C1) \\ HEX2 &= \overline{C2} \cdot \overline{C1} \cdot \overline{C0} + \cdot \overline{C2} \cdot C1 \cdot C0 \\ HEX1 &= \overline{C2} \cdot \overline{C1} \cdot \overline{C0} + \cdot \overline{C2} \cdot C1 \cdot C0 \\ HEX0 &= \overline{C2} \cdot C0 \end{split}$$

C2	C1	C0	HEX6	HEX5	HEX4	HEX3	HEX2	HEX1	HEX0
0	0	0	1	1	1	0	1	1	0
0	0	1	1	1	1	1	0	0	1
0	1	0	0	1	1	1	0	0	0
0	1	1	0	1	1	1	1	1	1
1	Χ	Χ	0	0	0	0	0	0	0

Figure 2: decoder truth table

Finally the logic states are implemented using gates as shown in *figure*3. The circuit is then described into VHDL using a dataflow style approach, the VHDL file is called *puntoA.vhd*.

The VHDL entry has been finally simulated via *testbenchapproach* where every possible input combination has been considered validating the output. The testbench results are shown below in figure 4.

Lab 02

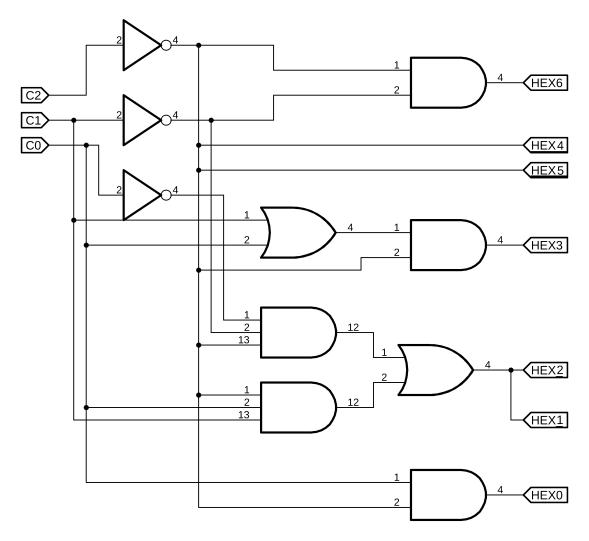


Figure 3: decoder gates implementation



Figure 4: Testbench results

2 Multiplexing the 7-segments display output

Figure 5 shows......

explanation

Lab 02

 


Figure 5: multiplexer + shifter + 7-segment decoder + display

3 Binary to Decimal converter

punto 3

4 Binary-to-BCD Converter

punto 4