



POLITECNICO DI TORINO

DIGITAL SYSTEMS ELECTRONICS  
A.A. 2018/2019

PROF. G. MASERA

---

## Lab 02

24 Mar 2019

---

Berchialla Luca	236032
Laurasi Gjergji	238259
Mattei Andrea	233755
Lombardo Domenico Maria	233959

# 1 Controlling a 7-segments display

Figure 1 shows a 7-segment decoder module whose input bits  $C_2C_1C_0$  drive a 7 segment display through the bits  $HEX0_0 \rightarrow HEX0_6$

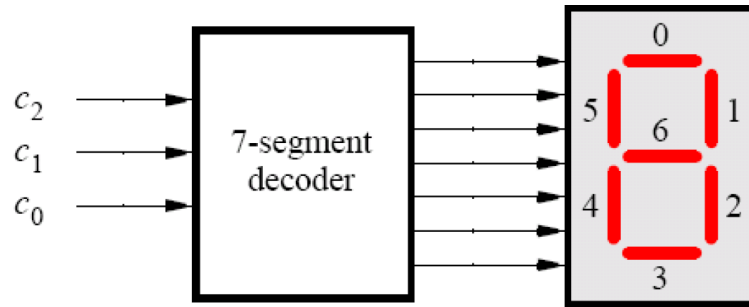


Figure 1: 7-segment decoder + display

Figure 2 shows the truth table to be implemented for the 7-segment decoder. As shown just the characters *HELO* will be implemented. The sequent logical states can be easily derived from the table:

$$HEX6 = \overline{C_2} \cdot \overline{C_1}$$

$$HEX5 = \overline{C_2}$$

$$HEX4 = \overline{C_2}$$

$$HEX3 = \overline{C_2} \cdot (C_0 + C_1)$$

$$HEX2 = \overline{C_2} \cdot \overline{C_1} \cdot \overline{C_0} + \overline{C_2} \cdot C_1 \cdot C_0$$

$$HEX1 = \overline{C_2} \cdot \overline{C_1} \cdot \overline{C_0} + \overline{C_2} \cdot C_1 \cdot C_0$$

$$HEX0 = \overline{C_2} \cdot C_0$$

C2	C1	C0	HEX6	HEX5	HEX4	HEX3	HEX2	HEX1	HEX0
0	0	0	1	1	1	0	1	1	0
0	0	1	1	1	1	1	0	0	1
0	1	0	0	1	1	1	0	0	0
0	1	1	0	1	1	1	1	1	1
1	X	X	0	0	0	0	0	0	0

Figure 2: decoder truth table

Finally the logic states are implemented using gates as shown in *figure3*.

The circuit is then described into VHDL using a dataflow style approach, the VHDL file is called *puntoA.vhd*.

The VHDL entry has been finally simulated via *testbenchapproach* where every possible input combination has been considered validating the output. The testbench results are shown below in figure 4.

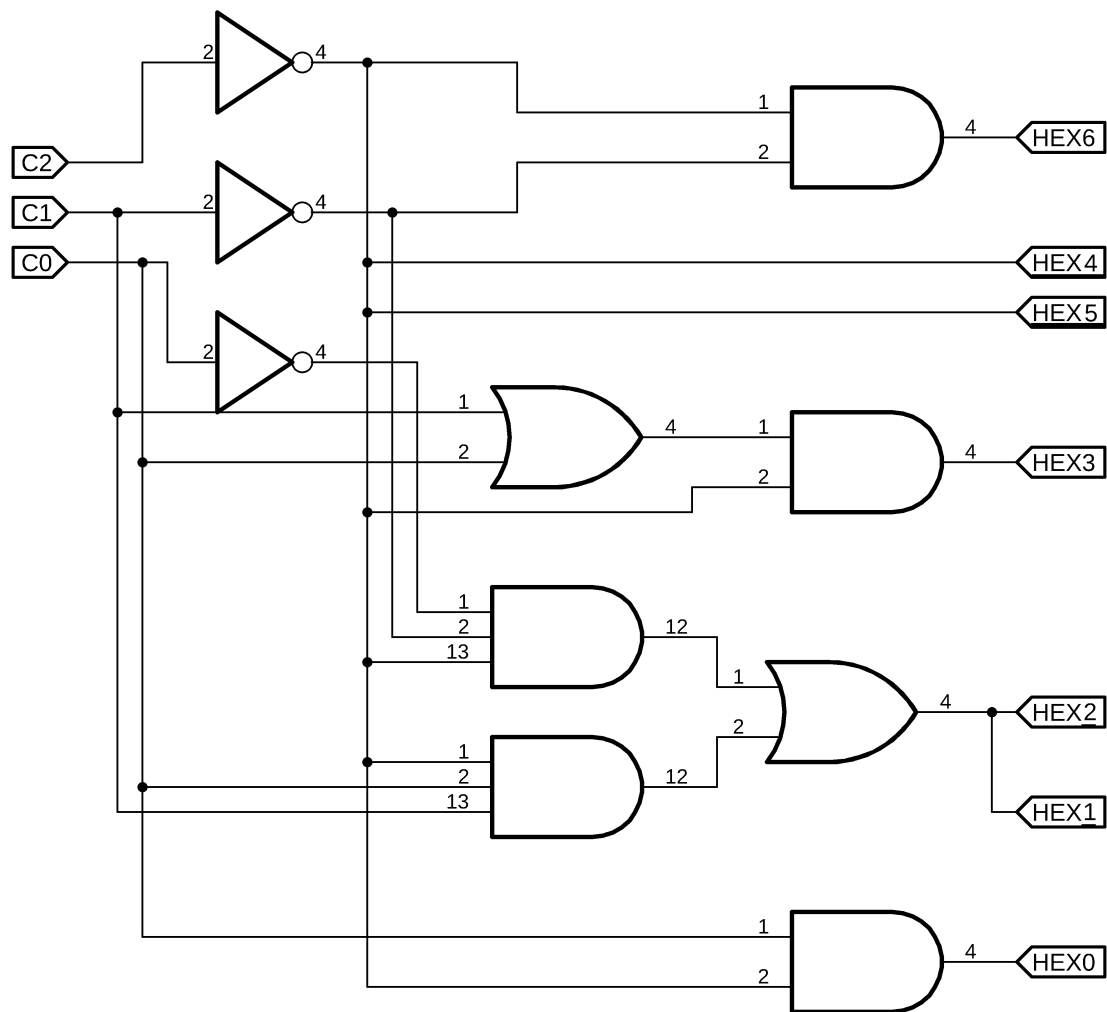


Figure 3: decoder gates implementation

/testbench/inp	000	001	010	011	100	101	110	111		
/testbench/outp	1110110	1111001	0111000	0111111	0000000					

Figure 4: Testbench results

- 2 Multiplexing the 7-segments display output
- 3 Binary to Decimal converter
- 4 Binary-to-BCD Converter